

# Homework 3 - COMP2020

Student name: Nguyen Tuan Anh

Student ID: V202100512

## Question 1

We will choose the Binary Encoding scheme as:

- Init: 00
- X1: 01
- X1-X2: 10
- X1-X2-X2: 11

From the FSM, we can have the following truth table:


Current State		Input		Next State		Output
s1	s0	i1	i0	s1n	s0n	
0	0	0	0	0	0	0
0	0	0	1	0	0	0
0	0	1	0	0	1	0
0	0	1	1	0	0	0
0	1	0	0	0	1	0
0	1	0	1	1	0	0
0	1	1	0	0	0	0
0	1	1	1	0	0	0
1	0	0	0	1	0	0
1	0	0	1	1	1	1
1	0	1	0	0	0	0
1	0	1	1	0	0	0
1	1	0	0	1	1	1
1	1	0	1	1	1	1
1	1	1	0	1	1	1
1	1	1	1	0	0	0

We can write the binary equation for  $s_{0n}$  and  $s_{1n}$  as:

$$s_{0n} = \bar{s}_1 \bar{s}_0 i_1 \bar{i}_0 + \bar{s}_1 s_0 \bar{i}_1 \bar{i}_0 + s_1 \bar{s}_0 \bar{i}_1 i_0 + s_1 s_0 (\bar{i}_1 \bar{i}_0 + \bar{i}_1 i_0 + i_1 \bar{i}_0)$$


$$s_{1n} = \bar{s}_1 s_0 \bar{i}_1 i_0 + s_1 \bar{s}_0 \bar{i}_1 \bar{i}_0 + s_1 \bar{s}_0 \bar{i}_1 i_0 + s_1 s_0 (\bar{i}_1 \bar{i}_0 + \bar{i}_1 i_0 + i_1 \bar{i}_0)$$

We can implement the circuit like this:

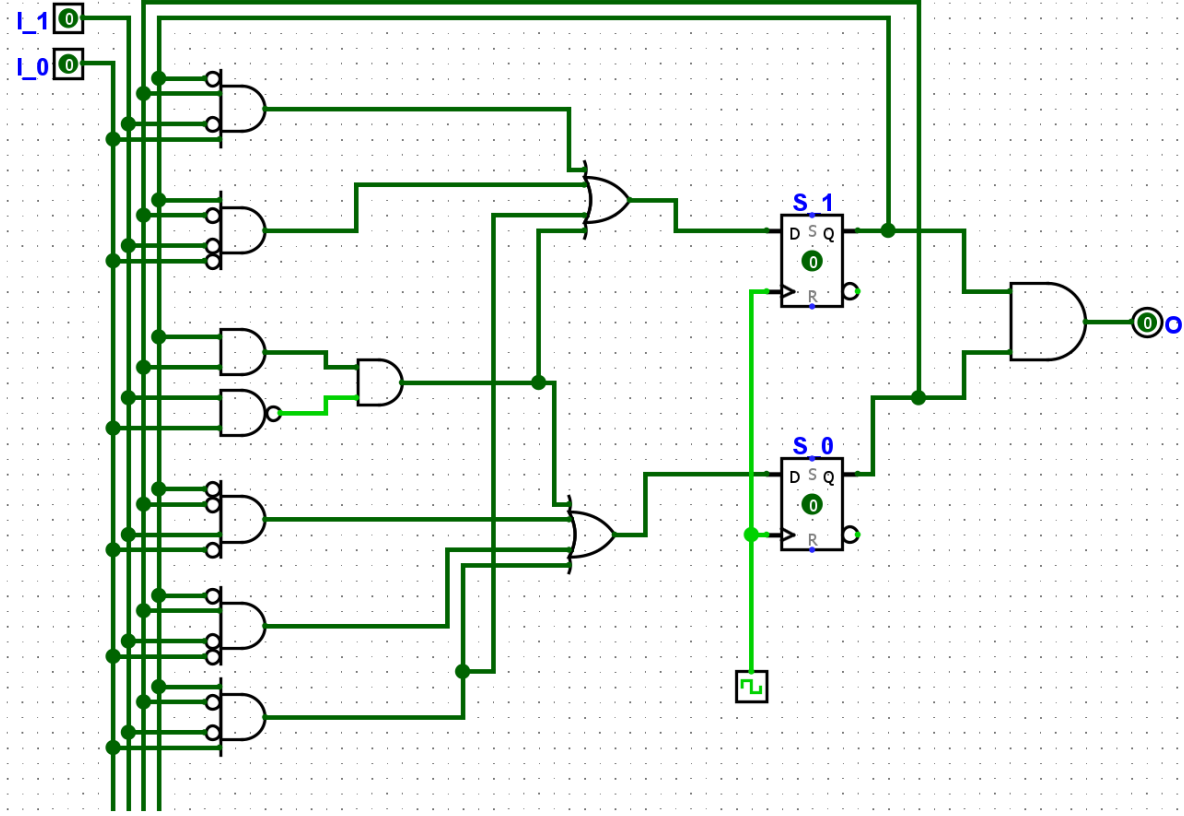
 
## Question 2

For the sequence detector, we have this FSM:



Also, we have this truth table:


State	Input		Output
S	1	0	O
00001	00010	00001	0
00010	00010	00100	0
00100	01000	00001	0
01000	10000	00100	0
10000	00010	00100	1

We can write the binary equation for every state  $s_{xn}$ : (the output)

$$\begin{aligned}
 s_{0n} &= \bar{i} \cdot (s_0 + s_2) \\
 s_{1n} &= i \cdot (s_0 + s_1 + s_4) \\
 s_{2n} &= \bar{i} \cdot (s_1 + s_3 + s_4) \\
 s_{3n} &= i \cdot s_2 \\
 s_{4n} &= i \cdot s_3
 \end{aligned}$$


Where  $s_0, s_1, s_2, s_3, s_4$  is the current state, and  $i$  is the input.

We can implement the circuit as:

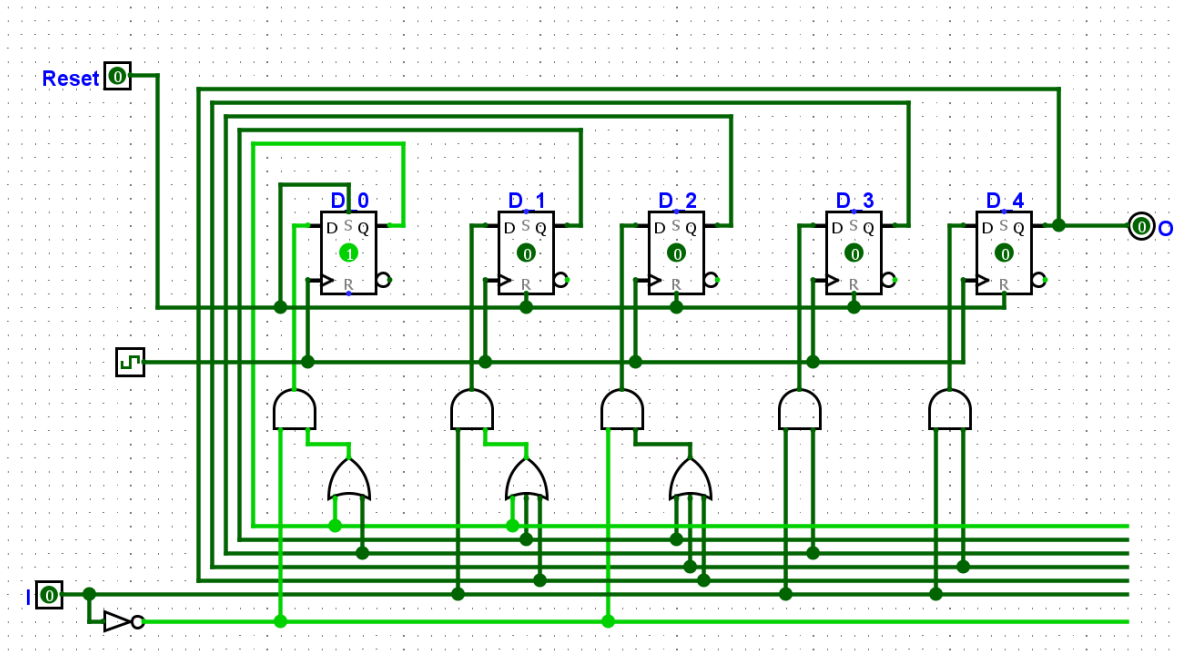
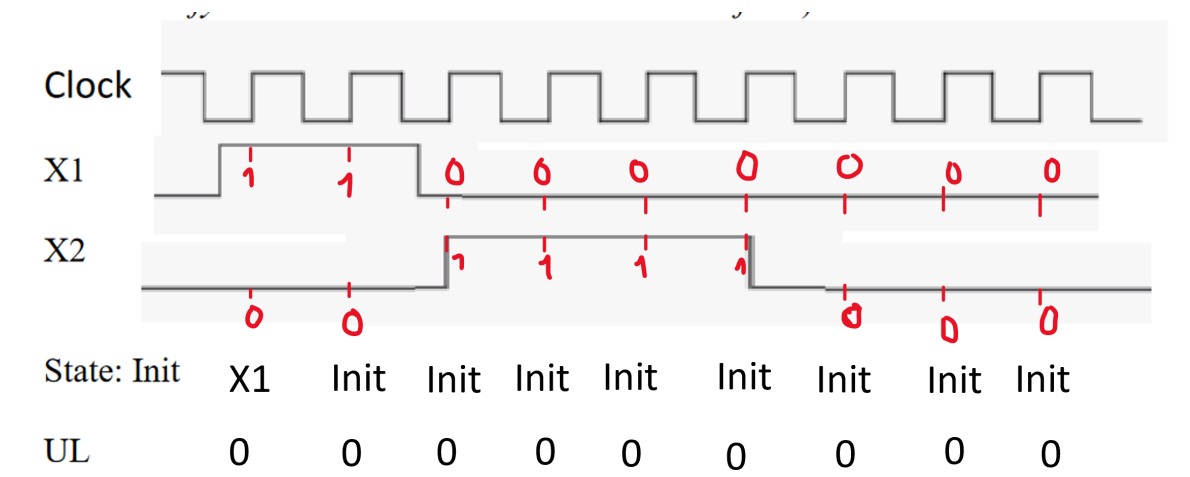
### Question 3

Assume the signal will be received on rising edge of the clock. We have the following result:



## Question 4

This register file supports 16 8-bit registers, with one write port and two write ports.

About I/O Ports:

- **RW**: 1 for allowing write to the register, 0 for read-only.
- **Activate**: Activate the Decoder for selecting the registers to write.
- **Select\_Reg\_W**: 4-bit value to select 1/16 registers (0000 to 1111) to write.
- **Data**: The 8-bit value for parsing to a register, based on the choice of **Select\_Reg\_W**.
- **Select\_Reg\_R1**, **Select\_Reg\_R2**: Two 4-bit values for selecting the data from 1/16 registers.
- **Output\_Reg1**, **Output\_Reg2**: Two 8-bit values, come from the register that selected from **Select\_Reg\_R1** and **Select\_Reg\_R2**.

The mechanism of the register file:

- The register file stores data of registers in 16 D Flip-flop, with number of data bits is 8.
- **Write**: With the **RW** and **Activate** enabled, value from **Select\_Reg\_W** will be parsed by decoder to the selected register. The AND Gate is used for enabling write action to a register when both write mode and the signal to that register is on.
- **Read**: 16 values from D Flip-flops will be sent to a multiplexer. The output of multiplexer will be chosen based on our selection of **Select\_Reg\_Rx**. Duplicate this design twice and we have two read ports.

